

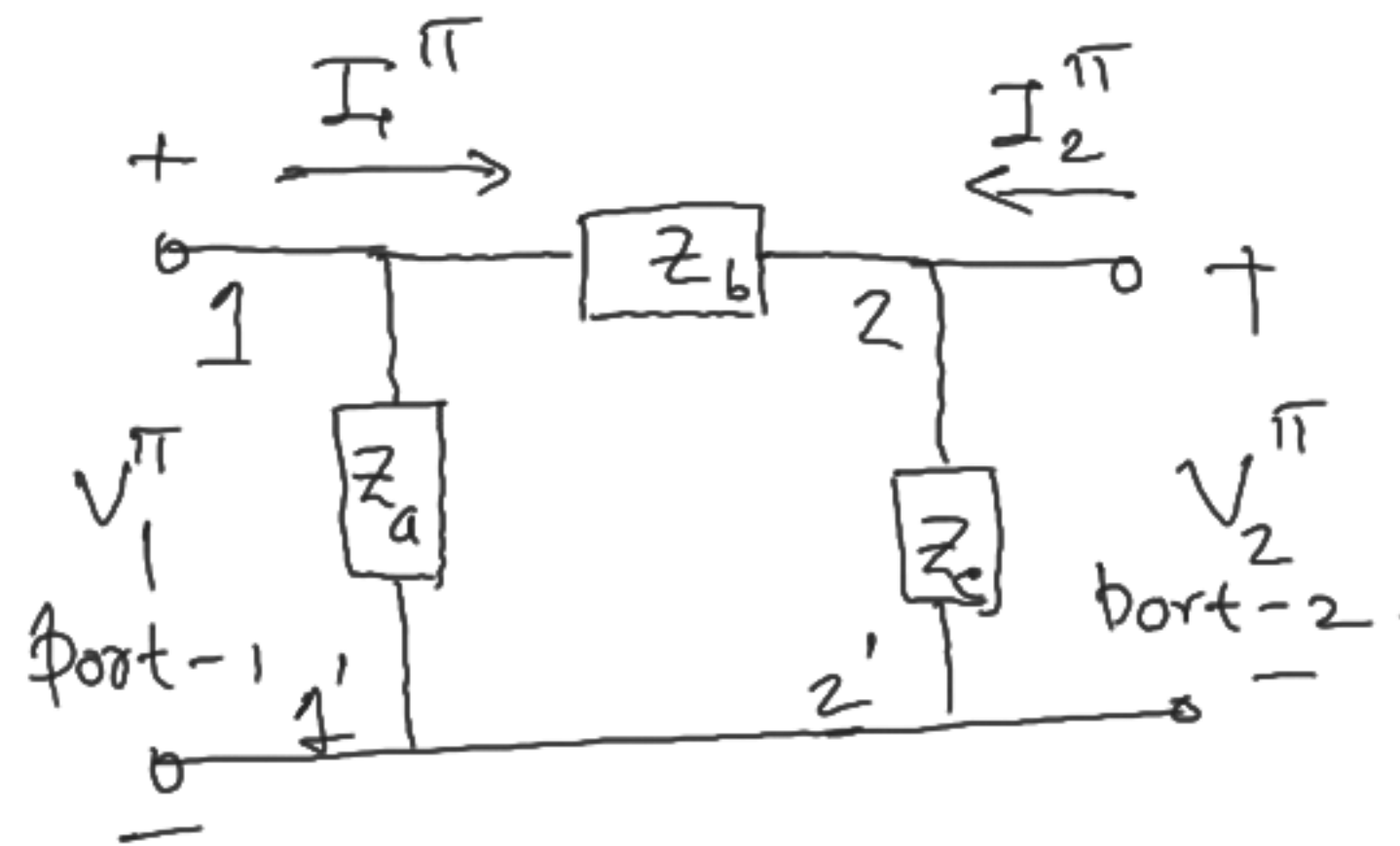


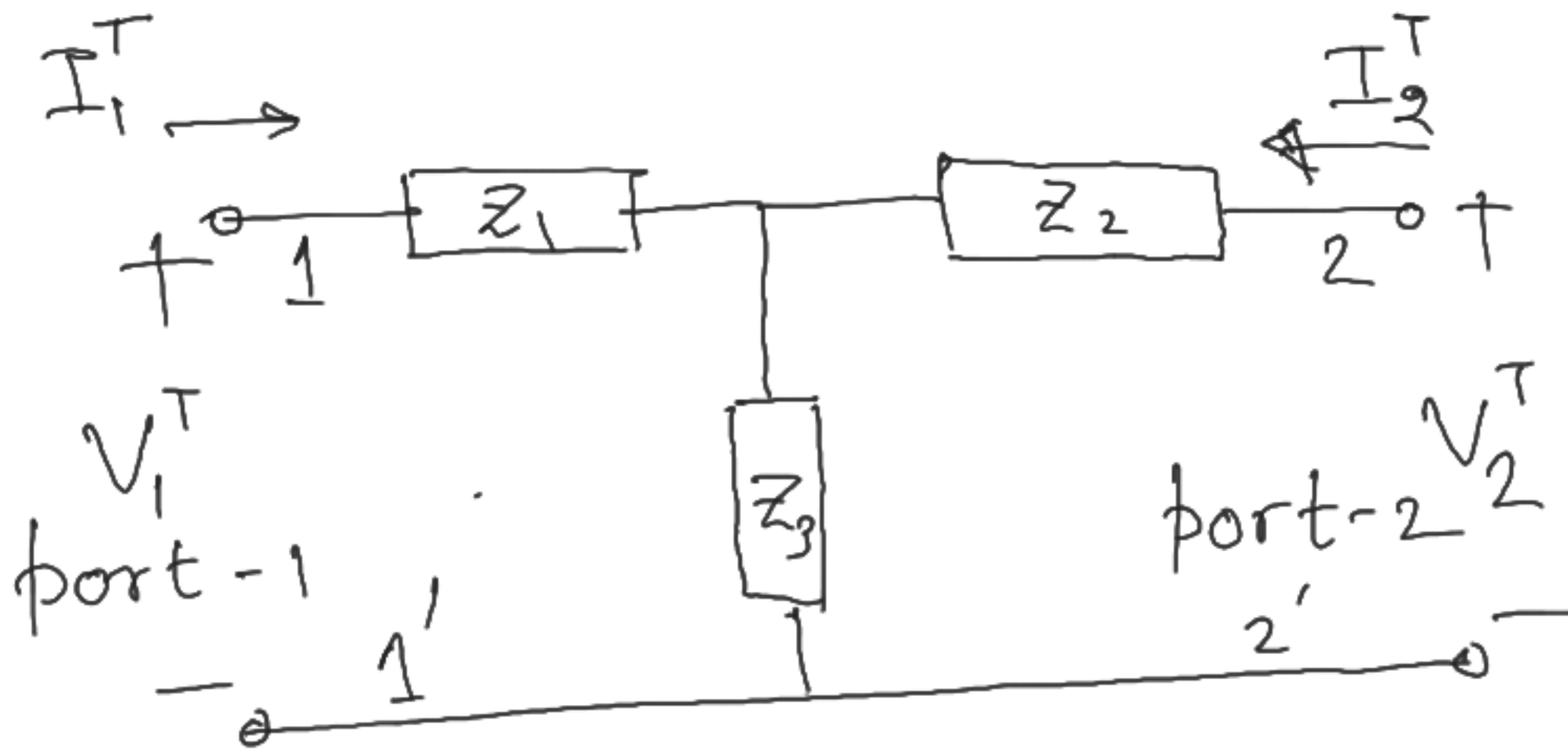
1. T- π network transformation (Star-delta transformation).



These two networks are equivalent if
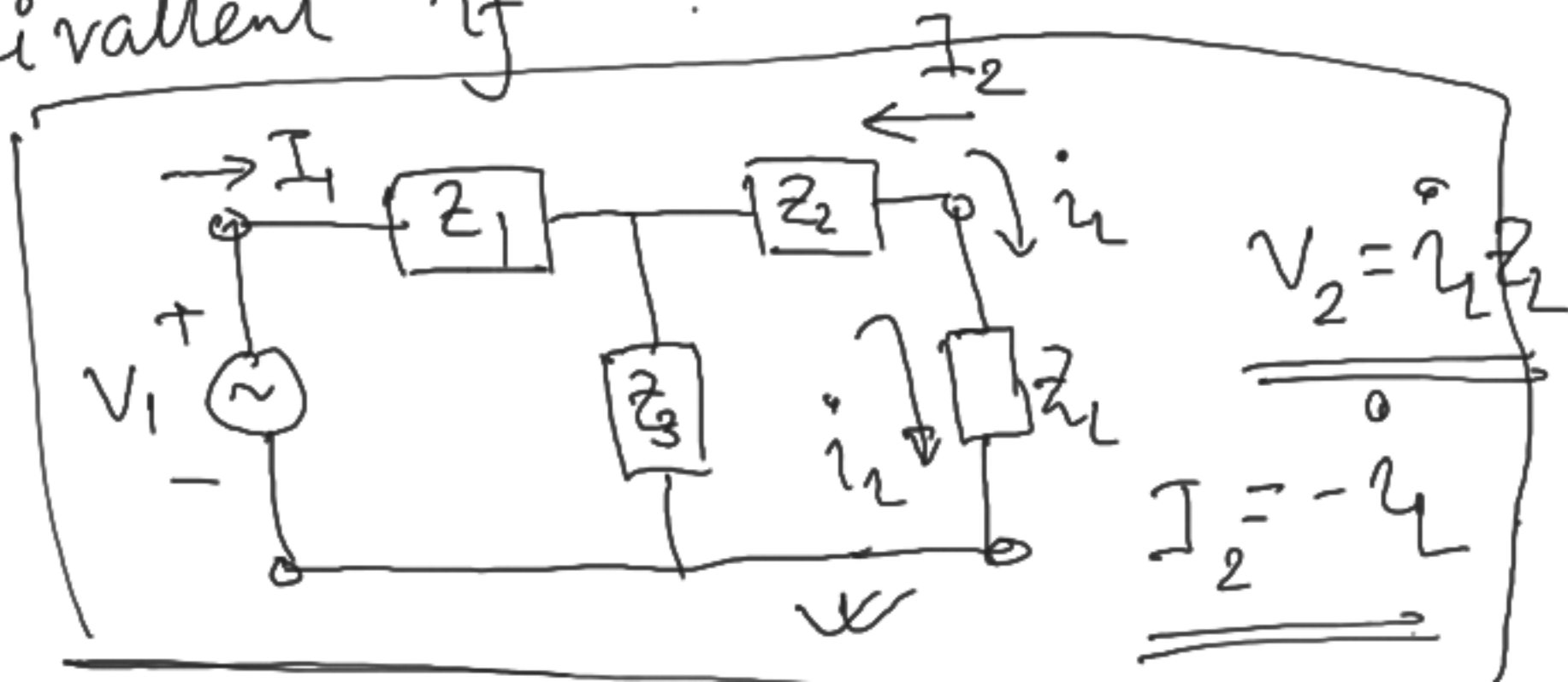
$$\left. \begin{aligned} V_1^T &= V_1^\pi ; & V_2^T &= V_2^\pi \\ I_1^T &= I_1^\pi ; & I_2^T &= I_2^\pi \end{aligned} \right\}$$




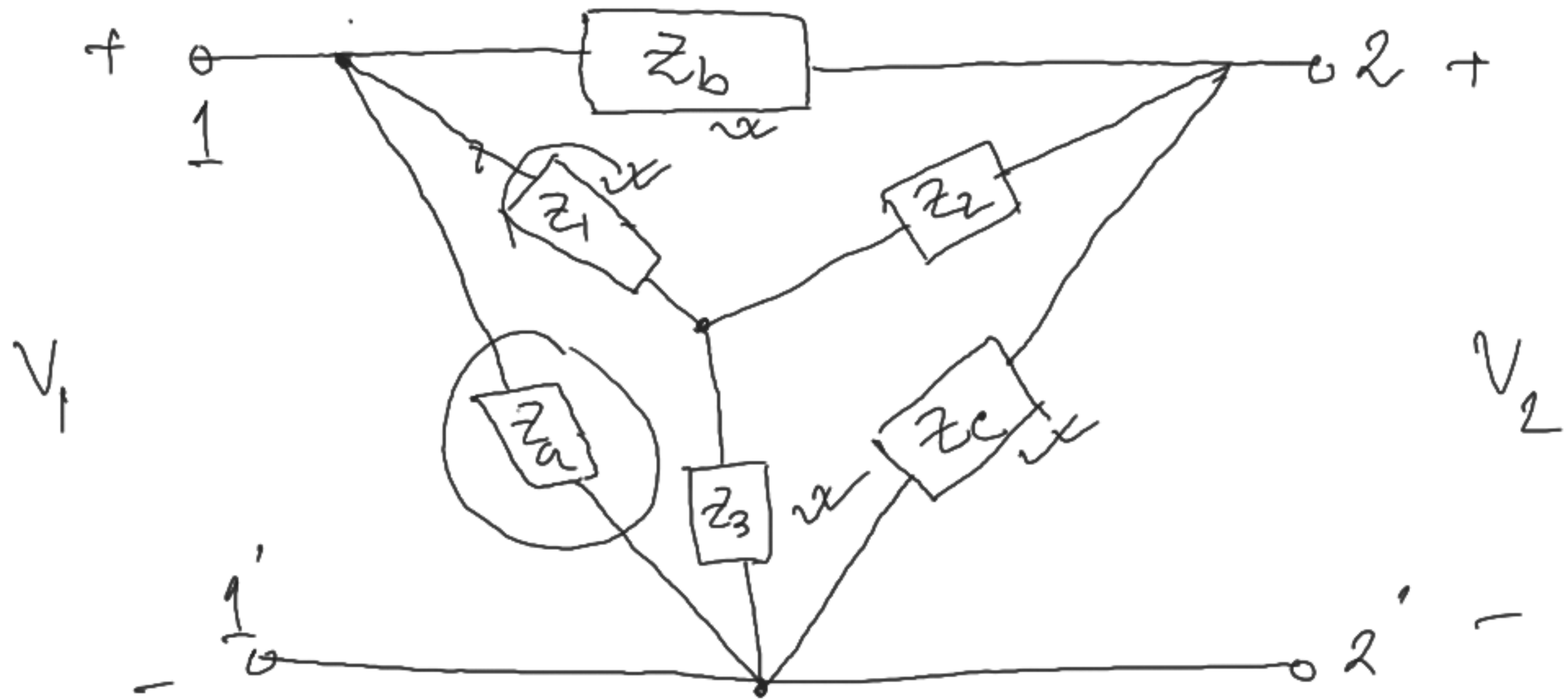

Ohm's law
 $\downarrow I \neq V$
KVL, KCL

Energy conservation

Charge conservation

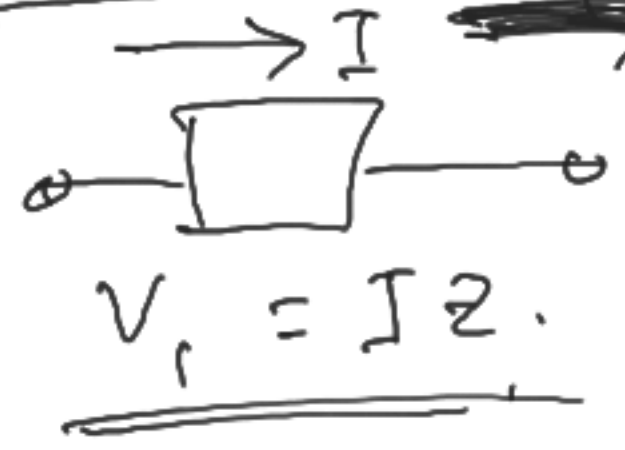

$$Z_1 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c}$$

$$Z_2 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c}$$

$$Z_3 = \frac{Z_a Z_c}{Z_a + Z_b + Z_c}$$

π to T conversion.

T to Π Conversion

T network impedances are z_1, z_2 and z_3 .

$$\left. \begin{aligned} z_A &= \frac{z_1 z_2 + z_2 z_3 + z_1 z_3}{z_2} \\ z_B &= \frac{z_1 z_2 + z_2 z_3 + z_1 z_3}{z_3} \\ z_C &= \frac{z_1 z_2 + z_2 z_3 + z_1 z_3}{z_1} \end{aligned} \right\}$$

2. Superposition Theorem


Statement: If a network of linear elements contains several independent energy sources, the total response is the sum of all the responses if each independent source acted separately and all other sources were replaced by their internal impedances.

Linear element: $I - V$ relation is linear.

$$\boxed{I \propto V.}$$

$$\boxed{I \propto V^{3/2}}$$






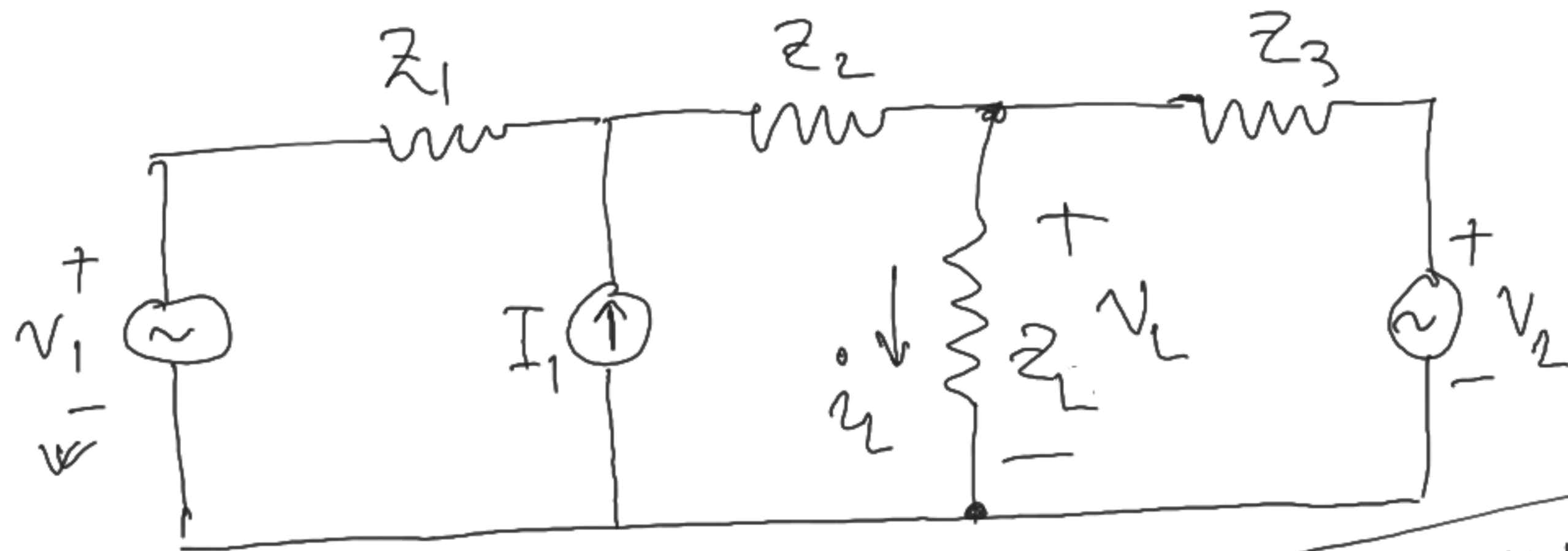



V_1 , I_1 and V_2 are independent:


$$V_L = V_1 + V_2 + V_3$$

$$V_L = i_1 Z_1 + i_2 Z_2 + i_3 Z_3$$

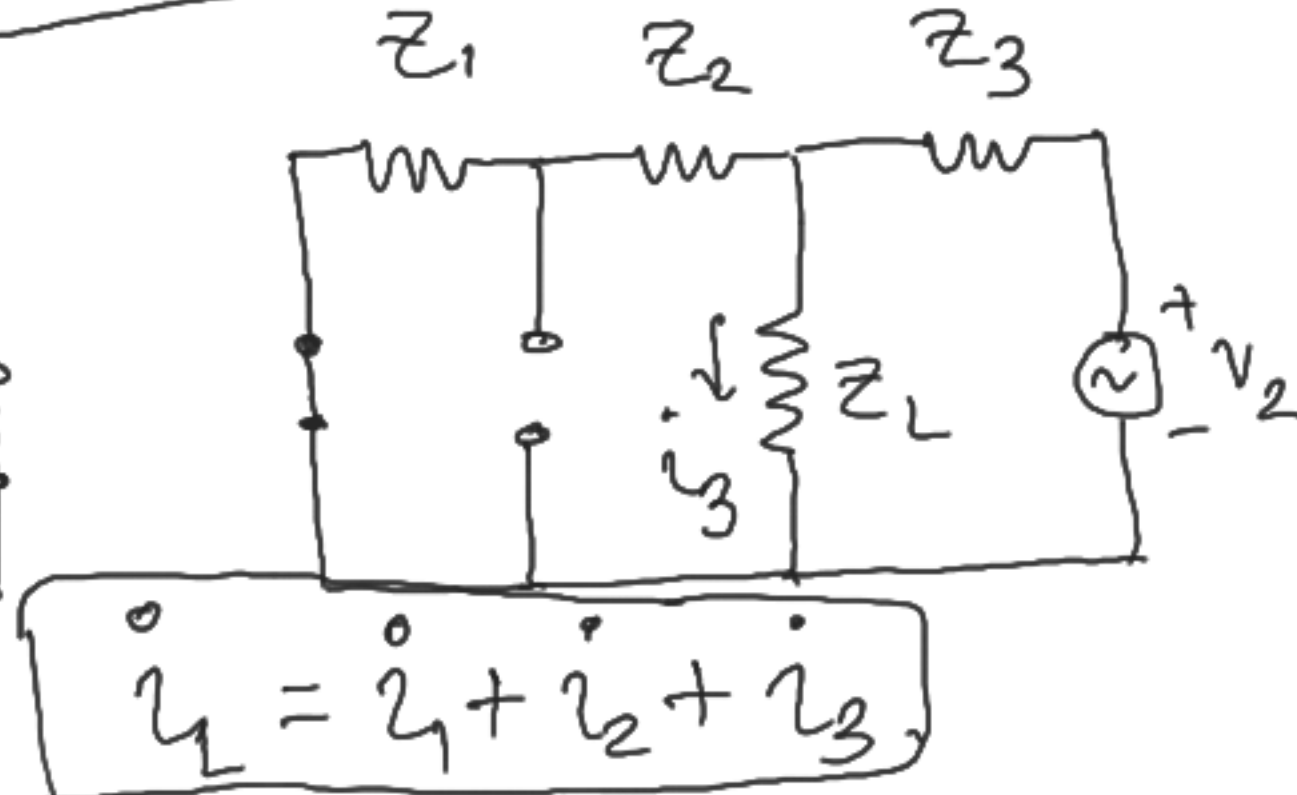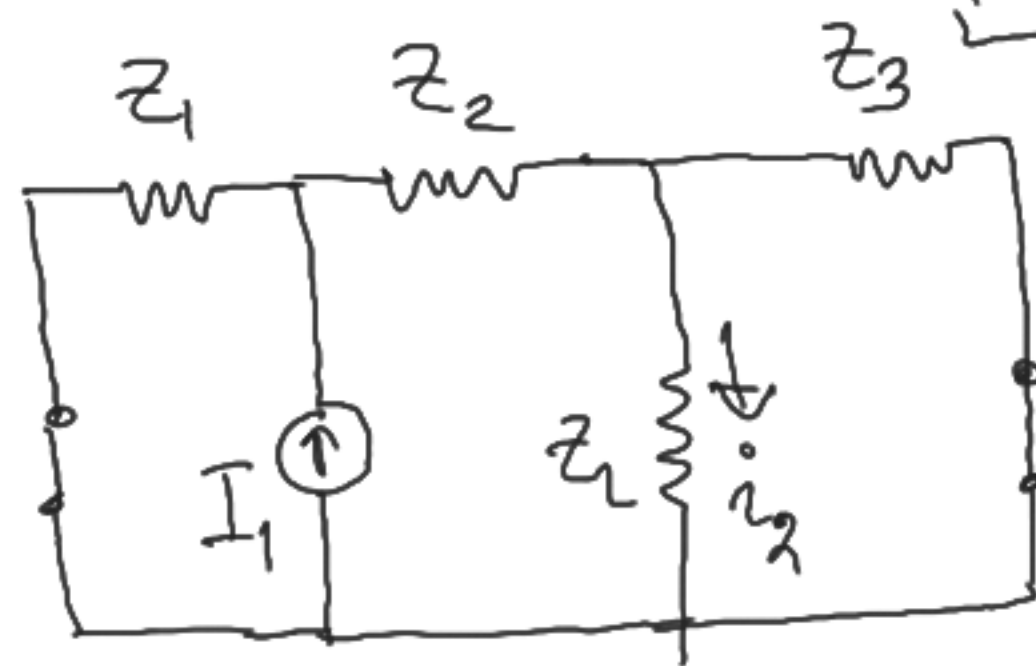
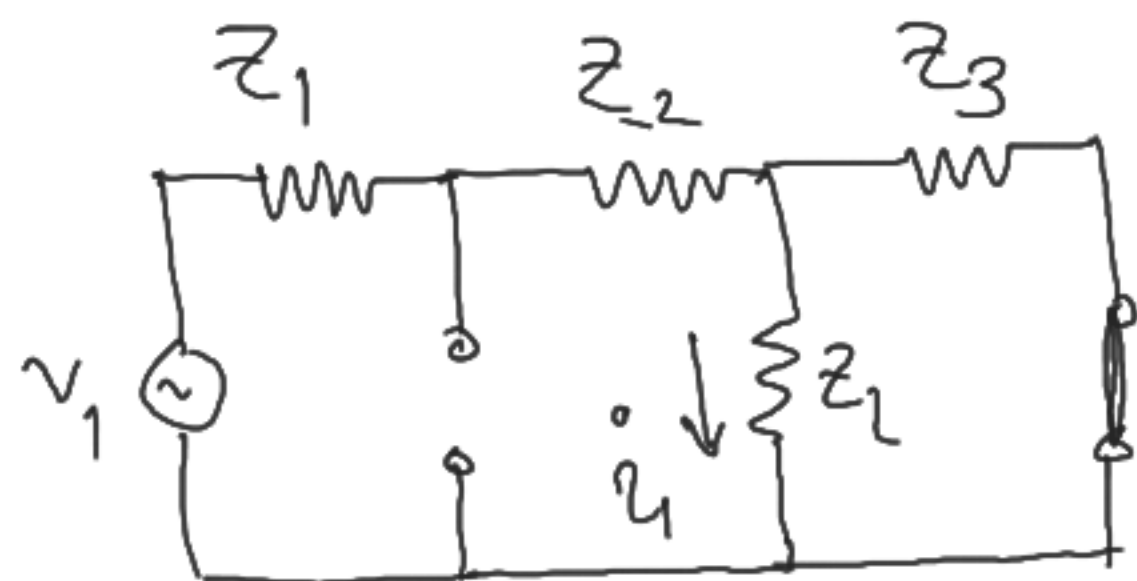


$$i_L = i_1 + i_2 + i_3$$

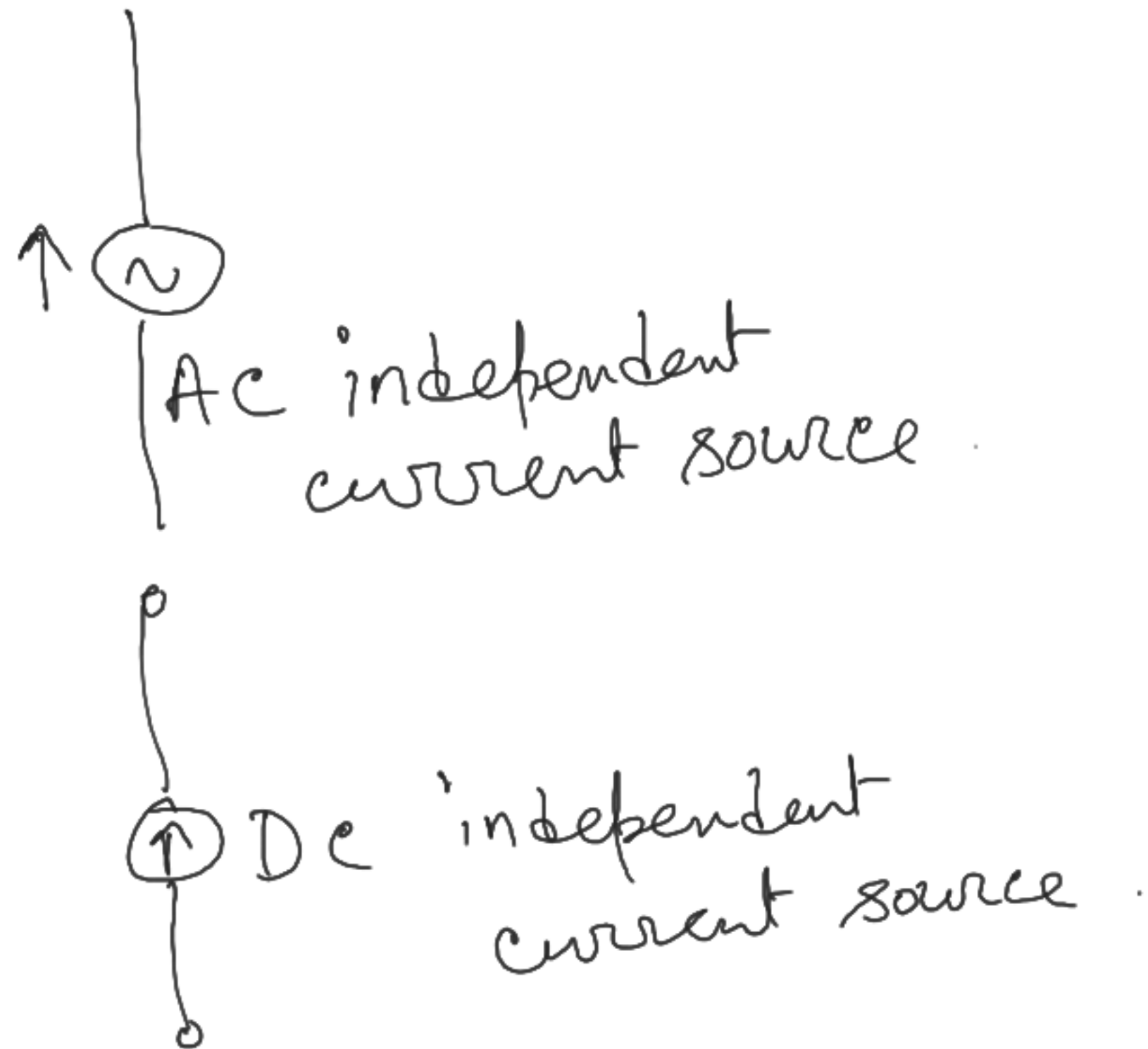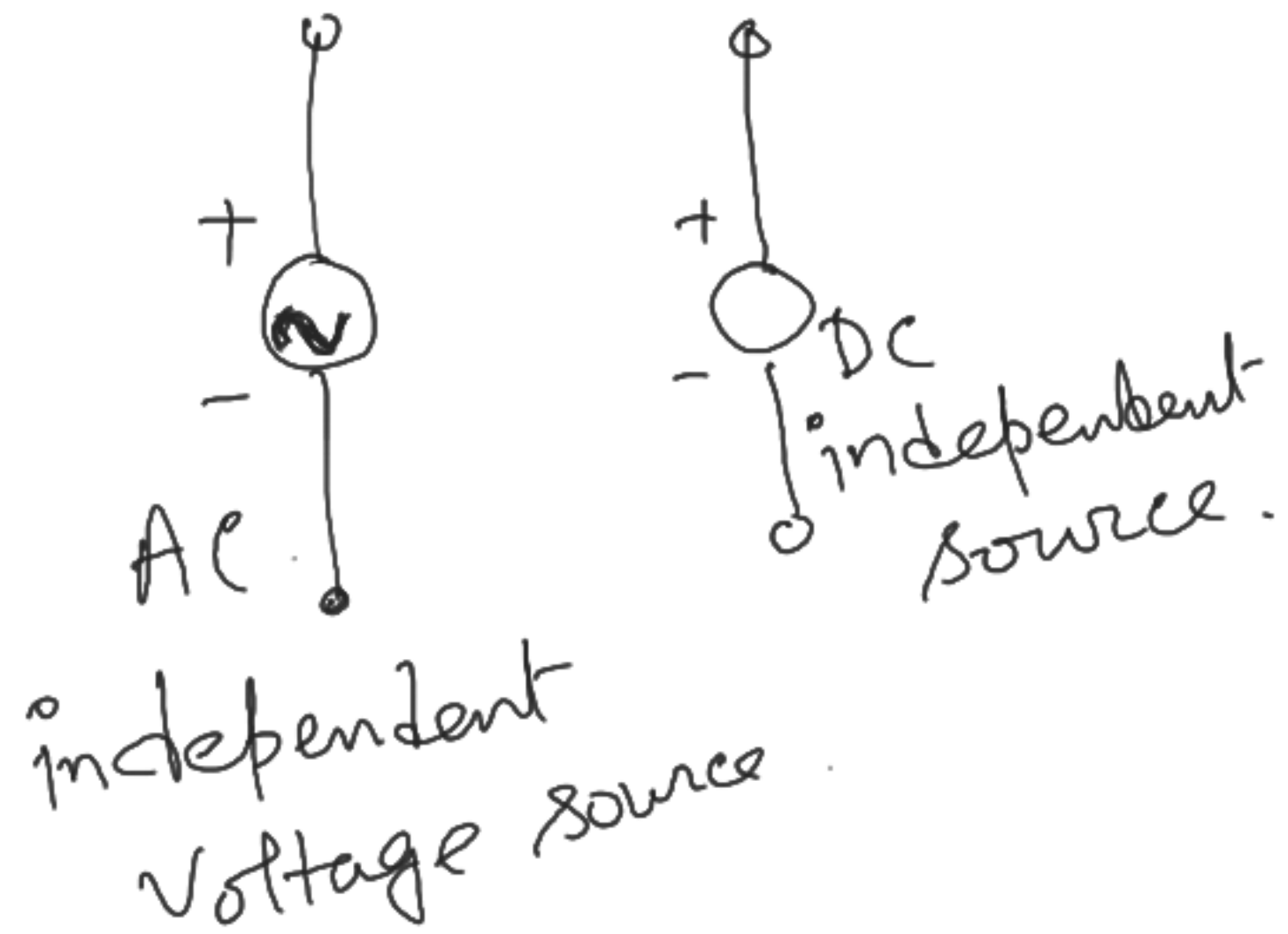


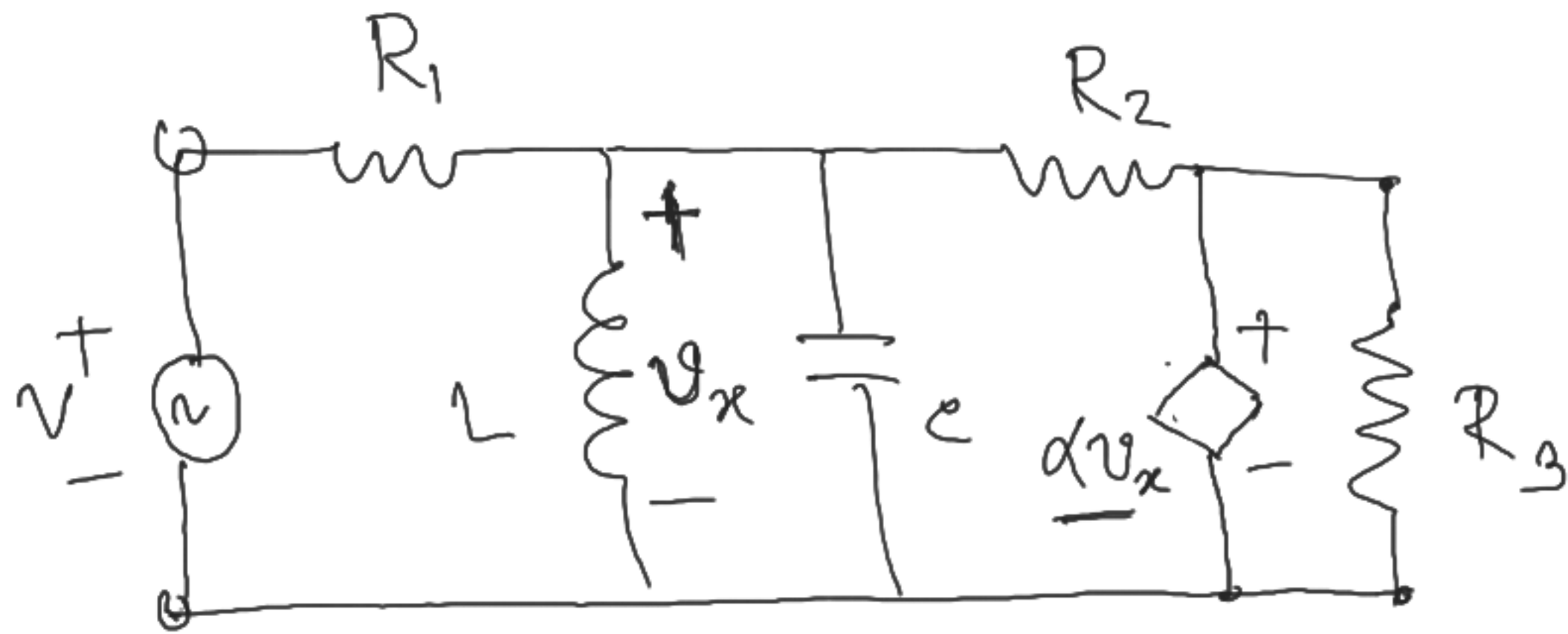

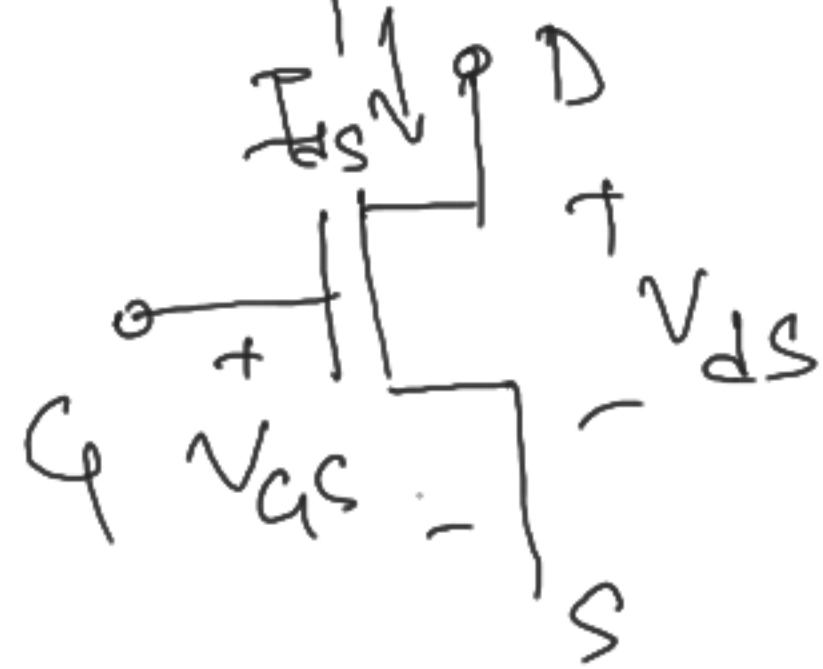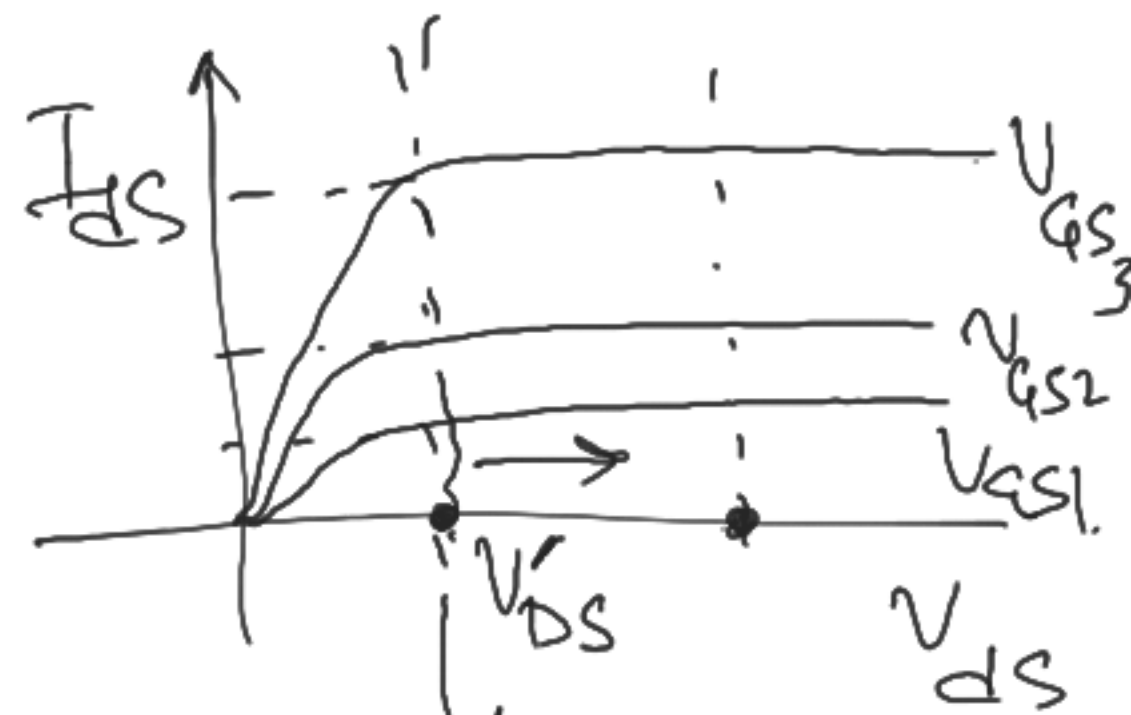* Current dependent current source α is a constant.
 ✓ Voltage dependent current source.
 ✓ Voltage dependent voltage source.



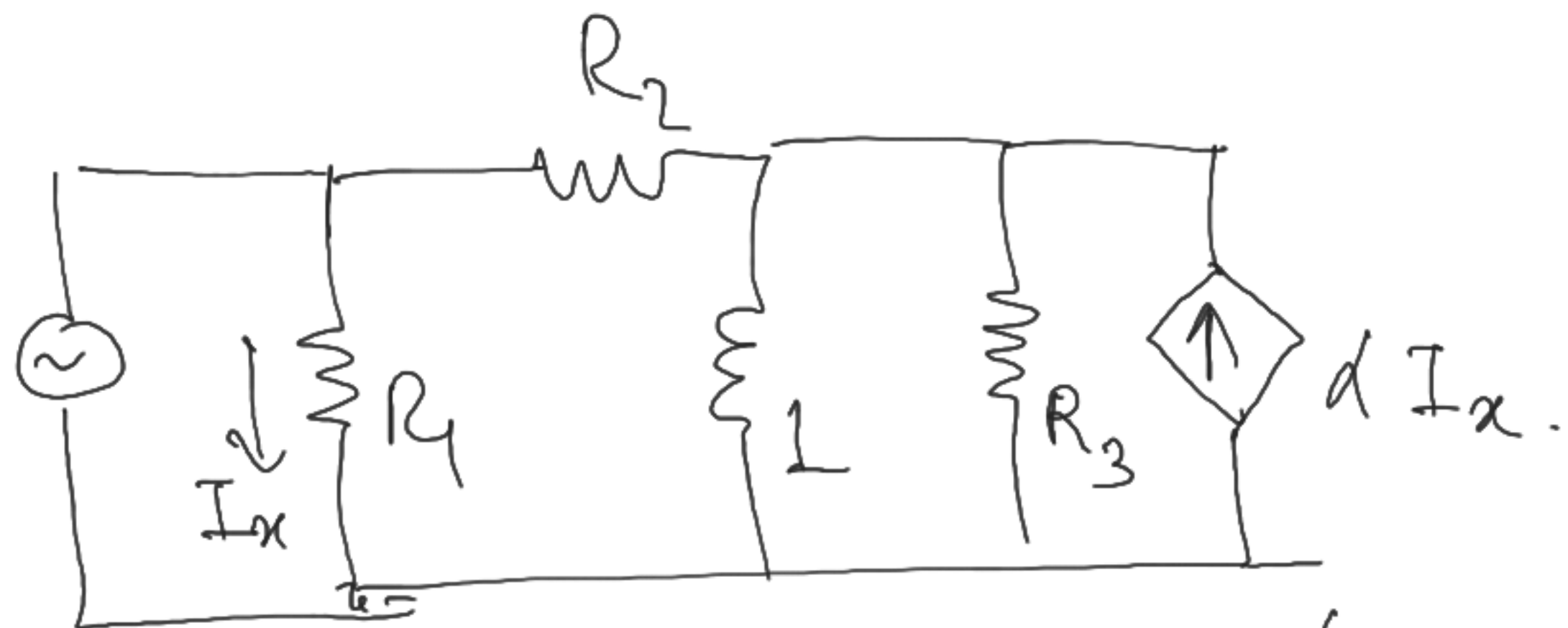$I_{ds} \Rightarrow f(V_{gs})$
 beyond V_{ds}



Current controlled (dependent) current source.
