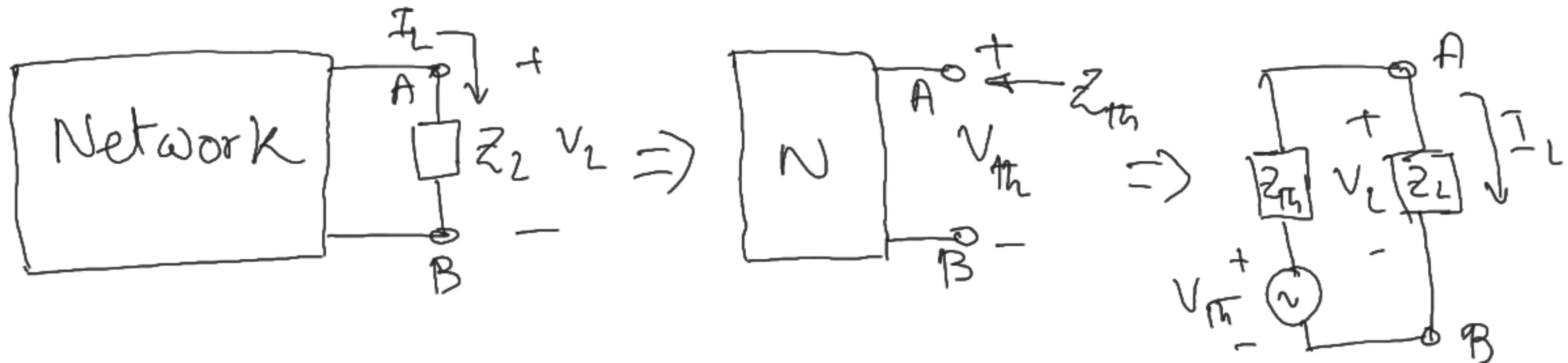



Thevenin's Theorem:

Any two terminal linear network containing impedances and sources may be replaced by a single independent source of voltage V_{th} and internal impedance Z_{th} .

Where V_{th} is the open circuit voltage at the terminal and Z_{th} is the impedance viewed at the terminal.




Norton's theorem

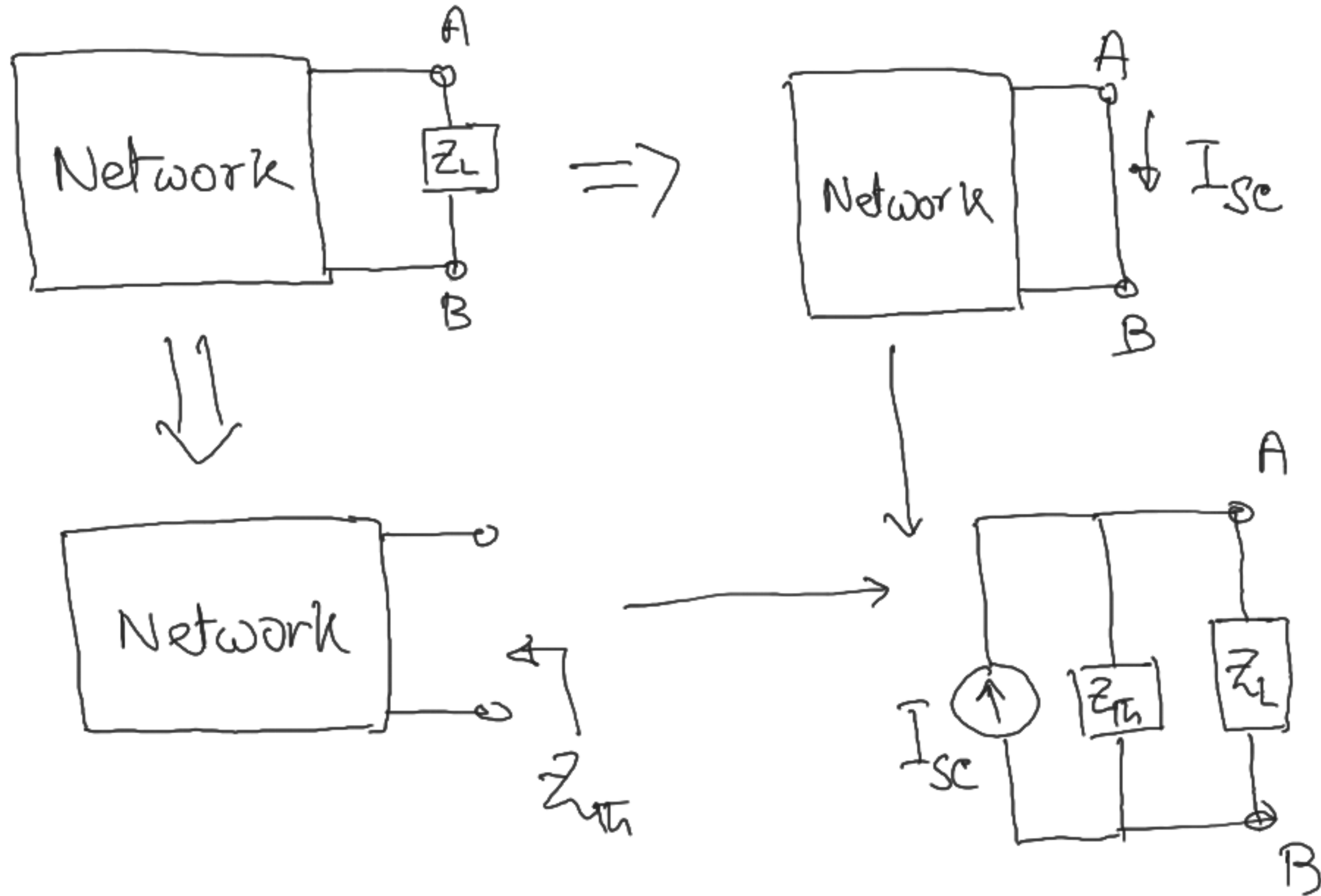

Compensation Theorem


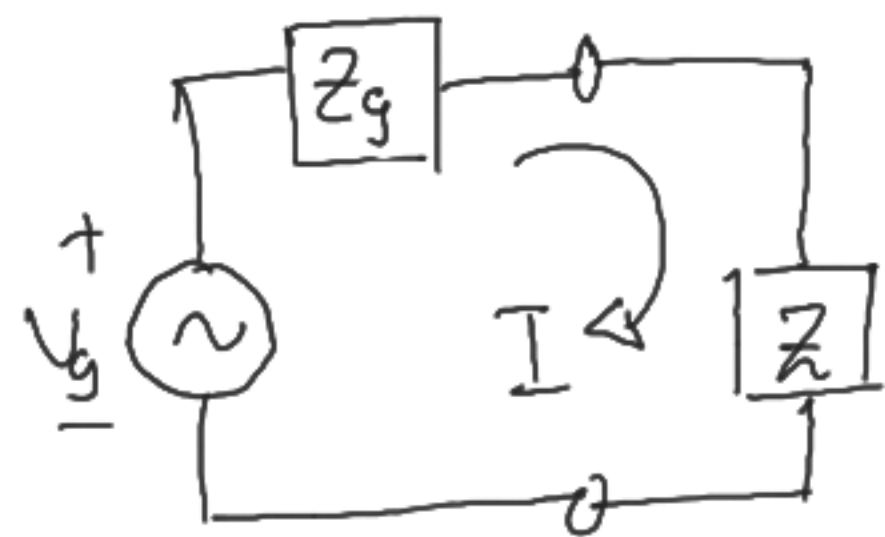
Statement: Consider a linear network in which an independent source is delivering current ' I ' to a load impedance Z . If Z is changed to $(Z + \delta Z)$. Then the change in current ' δI ' can be found by replacing the independent source by its internal impedance and placing a compensation voltage source has magnitude $V_c = I \delta Z$ and its polarity will oppose the current flow ' I '.



$$\delta I = I' - I = \frac{V_g}{(Z_g + Z + \delta Z)} - \frac{V_g}{(Z_g + Z)}$$

$$\delta I = I' - I = \frac{-V_g \delta z}{(z_g + z)(z_g + z + \delta z)} = -\frac{I \delta z}{z + z_g + \delta z}$$

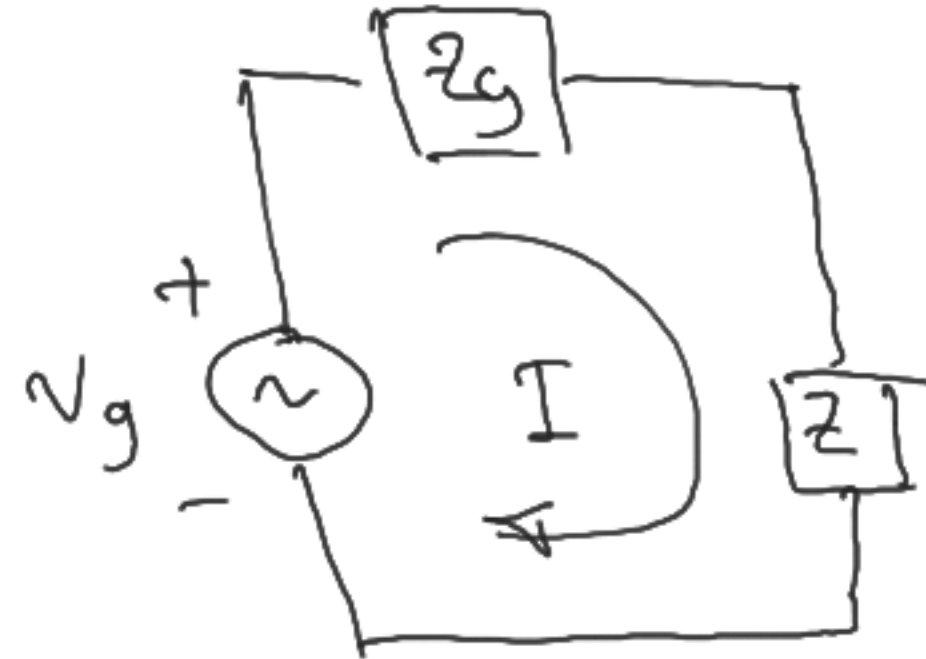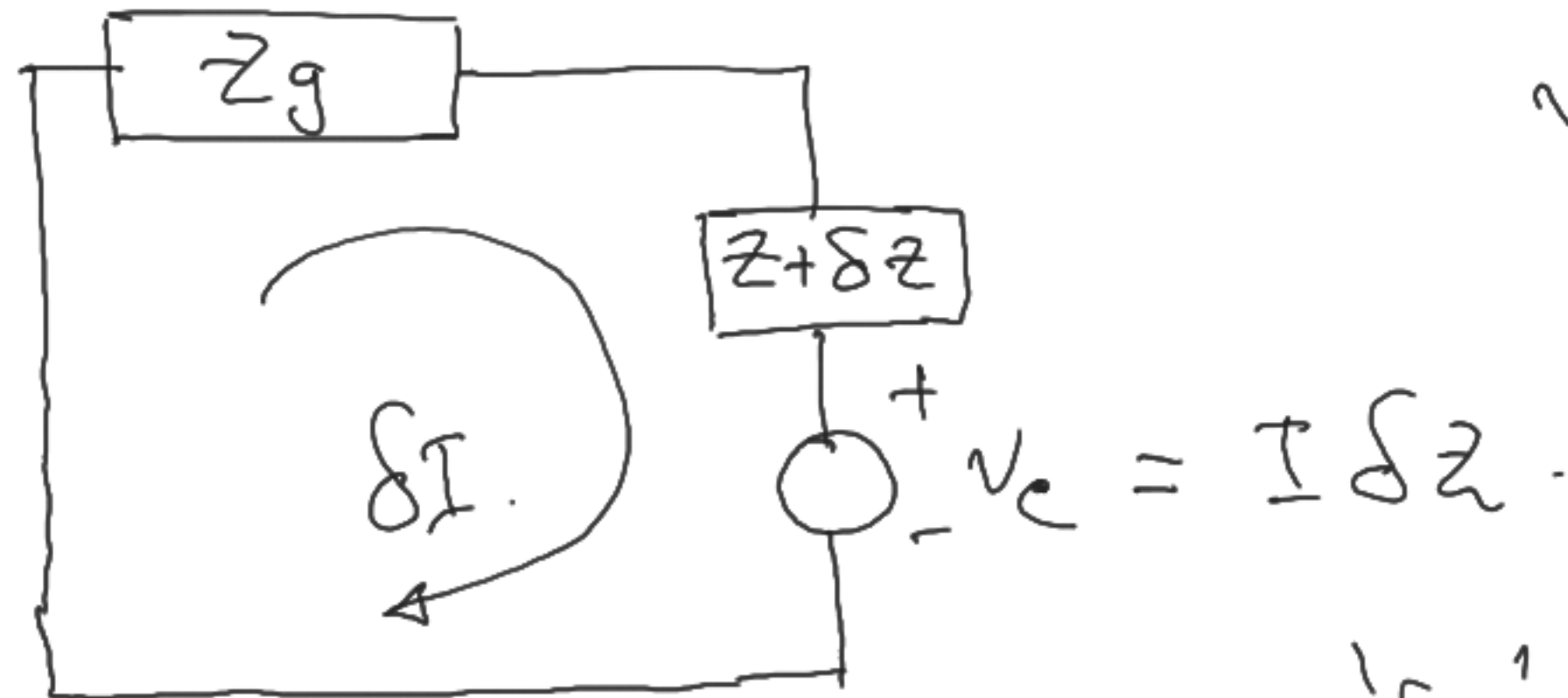
$$\delta I = -\left(\frac{V_c}{z + z_g + \delta z} \right)$$



' δz ' is the change in load impedance.

Millman's Theorem


$$Y = \frac{1}{Z}$$

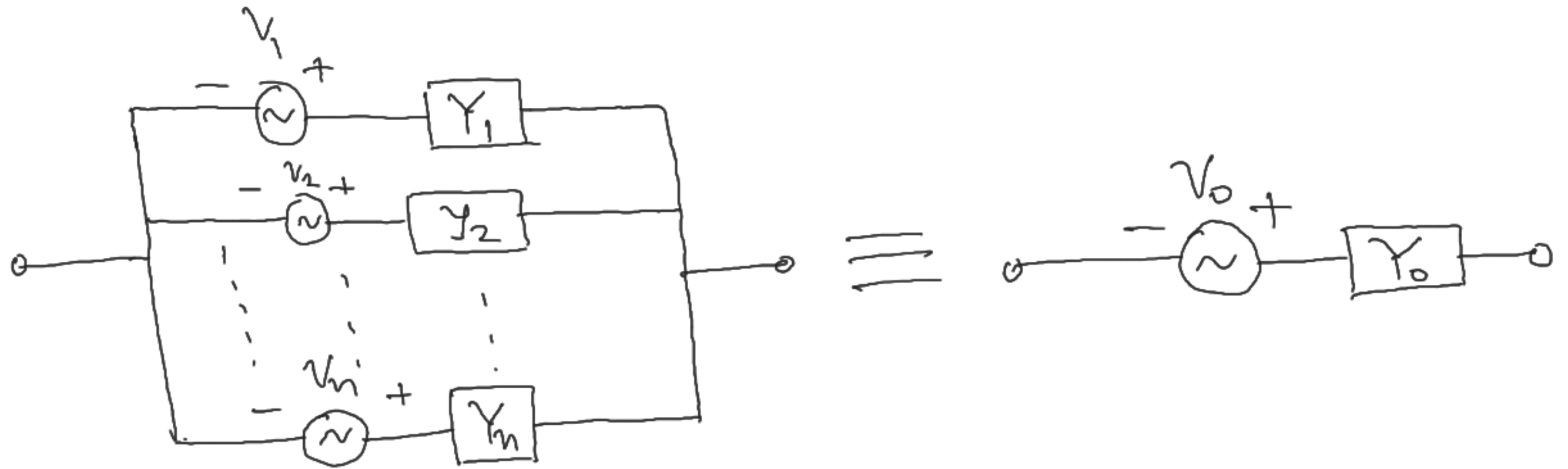

$$v_0 = \frac{v_1 Y_1 + v_2 Y_2 + \dots + v_n Y_n}{Y_1 + Y_2 + \dots + Y_n} = \frac{\sum_i v_i Y_i}{\sum_i Y_i}$$

$$Y_0 = Y_1 + Y_2 + \dots + Y_n = \sum_i Y_i$$

Maximum power transfer Theorem

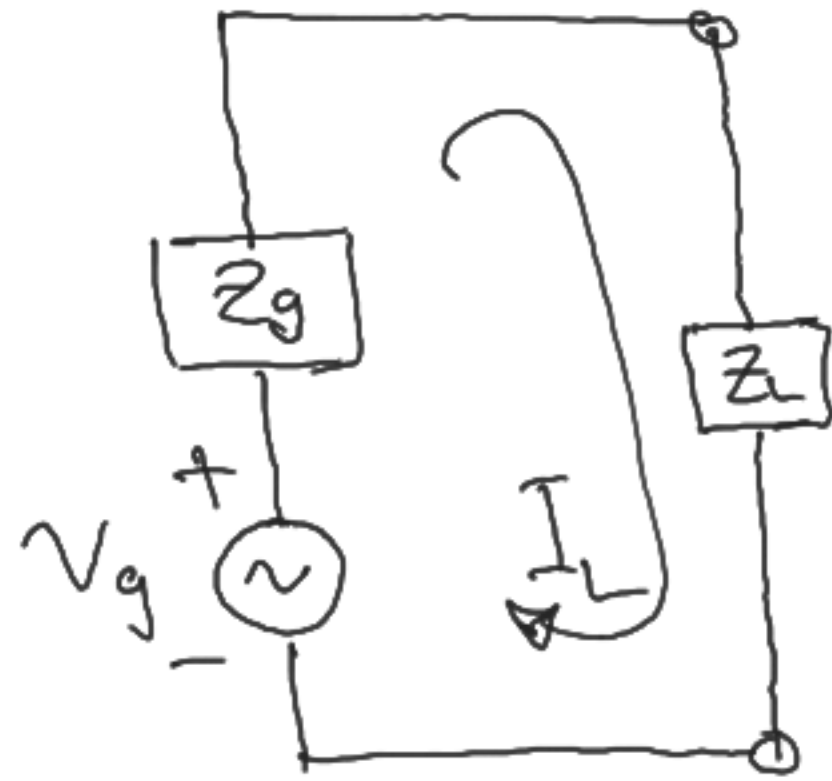

- i) Z_L is a pure resistance ($Z_L = R_L$).
 - ii) Z_L is combination of resistance & reactance. ($Z_L = R_L + jX_L$).
- ($Z_g = R_g$)
($Z_g = R_g + jX_g$)

i) $Z_L = R_L$ and $Z_g = R_g$:

$$I_L = \frac{V_g}{R_g + R_L}$$

Power delivered to the load (P_L) = $I^2 R_L = \left(\frac{V_g}{R_g + R_L} \right)^2 \cdot R_L$.

If the P_L is maximum then

$$\frac{dP_L}{dR_L} = 0.$$

$$\frac{dP_L}{dR_L} = \frac{V_g^2 [(R_L + R_g)^2 - 2R_L(R_L + R_g)]}{(R_L + R_g)^4} = 0.$$

$$R_L = R_g$$

$$P_{L, \max} = \frac{V_g^2}{4R}$$

Efficiency is 50%.

"Half power will be dissipated in the source resistance ' R_g '".

ii) $Z_g = R_g + jX_g$ and $Z_L = R_L + jX_L$:

$$I = \frac{V_g}{(R_L + R_g) + j(X_L + X_g)} ; \quad |I| = \frac{V_g^2}{(R_L + R_g)^2 + (X_L + X_g)^2}$$

Power delivered to the load $(P_L) = \underline{\underline{|I|^2 \cdot R_L}}$

$$P_L = \frac{V_g^2 R_L}{(R_L + R_g)^2 + \underline{(X_L + X_g)^2}}$$

for maximum power transfer by adjusting load reactance,

$\boxed{X_L = -X_g}$ can be set.

$$P_{L, \max}^x = \frac{V_g^2 R_L}{(R_L + R_g)^2}.$$

If $R_L = R_g$ Then $P_{L, \max}^x = P_{\max}.$

Therefore the conditions for maximum power transfer

$$\left. \begin{array}{l} \text{a. } X_L = -X_g \\ \text{b. } R_L = R_g \end{array} \right\}.$$

$$\boxed{Z_L = Z_g^*}$$