

Millman's Theorem.

$$\left\{ \frac{\frac{6}{2} + \frac{3}{1}}{\frac{1}{2} + \frac{1}{1}} = V_{eq1} = \frac{6}{3/2} \right.$$



$V_{eq1} = 4V.$

$$Y = \frac{1}{2} + 1 = \frac{3}{2}$$

$$R_{eq} = \frac{2}{3}$$

Reduce the circuit into a single voltage source and associated resistance.
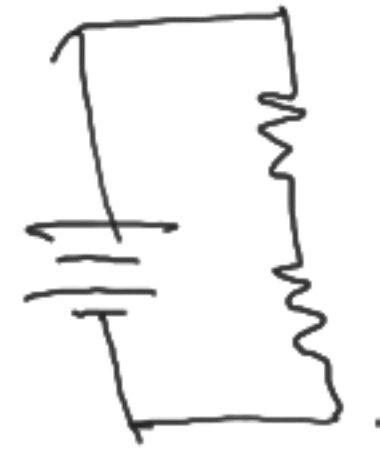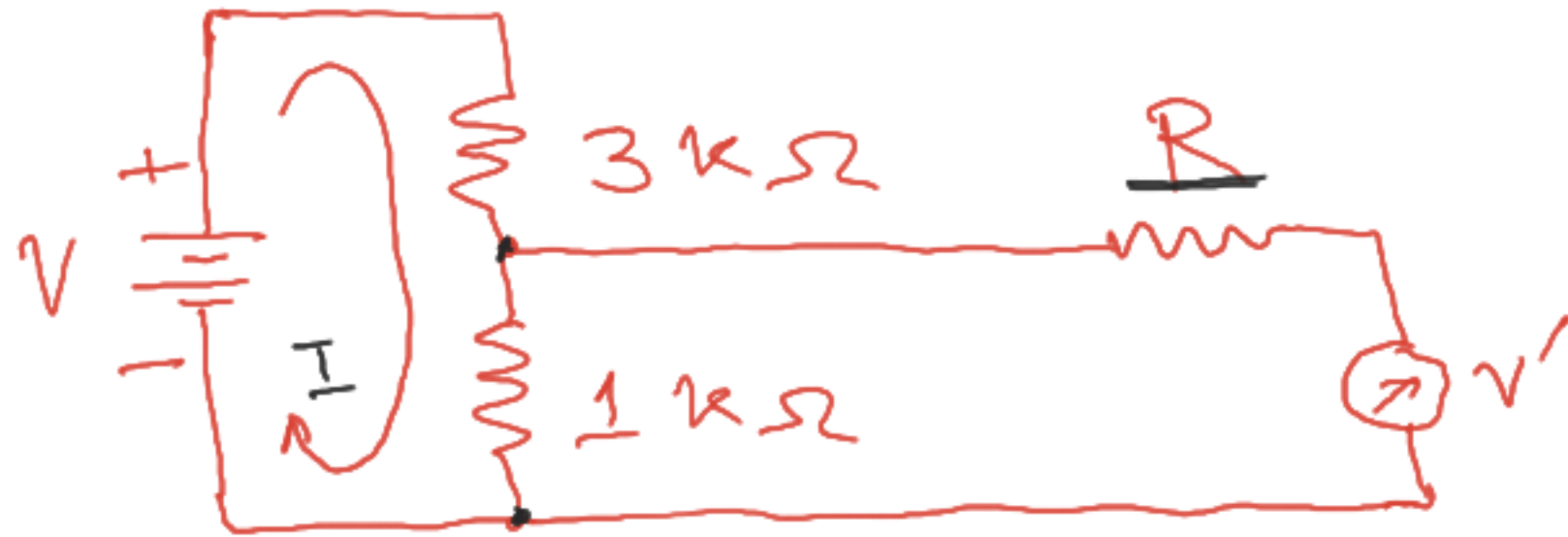
$$\Rightarrow \underline{I = \frac{4V}{3} \text{ mA}}$$



Using Thevenin's theorem, determine the lowest resistance which the voltmeter must have so that the measurement error shall not exceed 1%.



$$\underline{Z_{th} = R_{th} + jX_{th}}$$

The network (N) contains linear, passive, bilateral elements.

If $R_L = 1.5 \Omega$ then $I = 2A$.

If $R_L = 4 \Omega$ Then $I = 1A$.

Determine R_L for maximum power transfer.

$$V_{th} = I R_{th} + I R_L$$


$$V_{th} = 2 R_{th} + 2 \times 1.5$$

$$V_{th} = 2 R_{th} + 3 \dots (i)$$

$R_L = 1 \Omega$ for maximum power transfer

$$V_{th} = R_{th} + 4 \dots (ii)$$
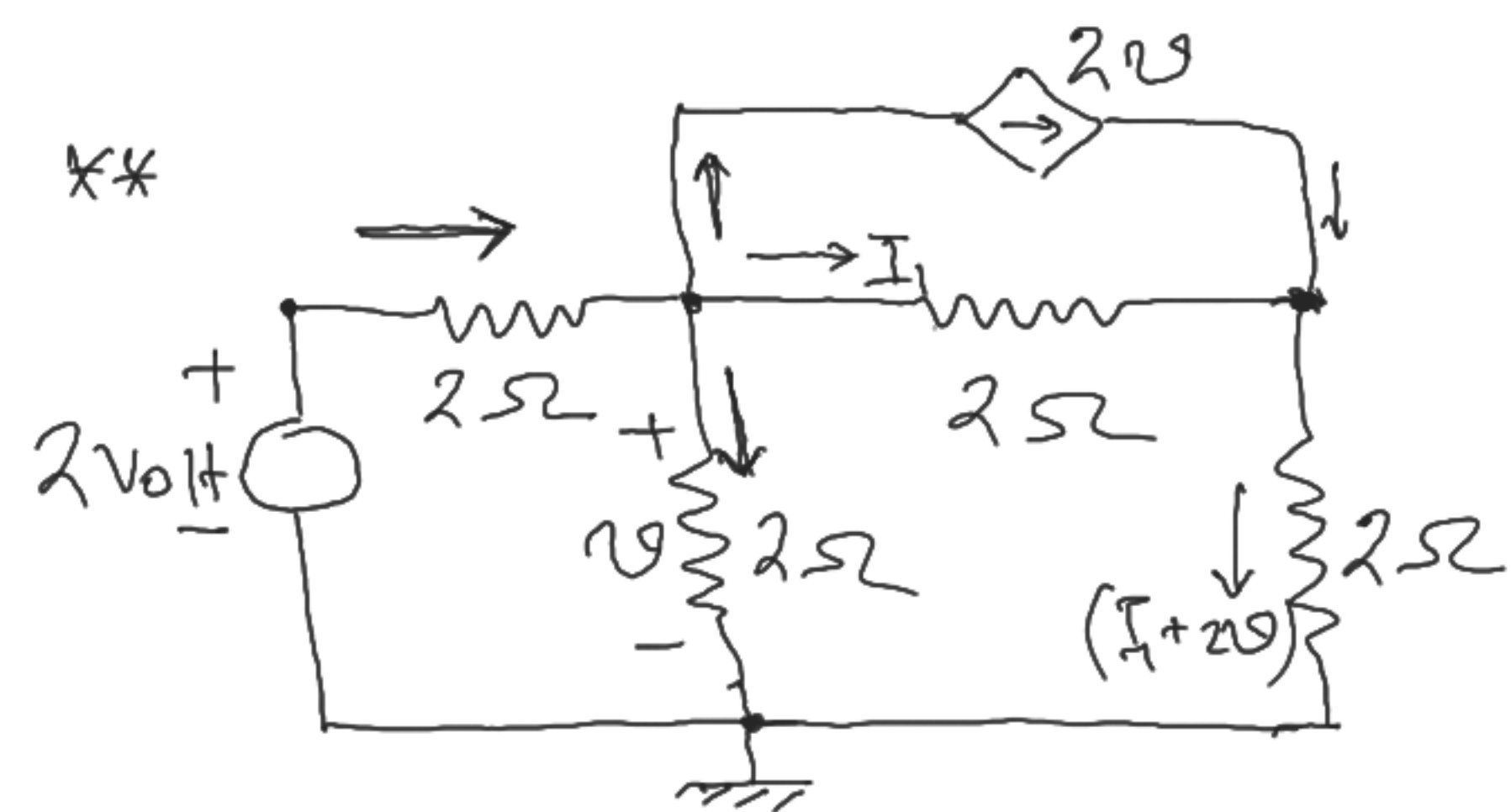
$$V_{th} = 5V \quad \& \quad R_{th} = 1 \Omega$$



Find out 'v'.

$$\Rightarrow \frac{2-v}{2} = \frac{v}{2} + I + 2v$$


$$6v + 2I_2 = 2 \dots\dots (i)$$

$$v = 2I_1 + 2(I_1 + 2v)$$

$$\boxed{I_1 = -\frac{3}{4}v} \dots\dots (ii)$$

From (i) & (ii)
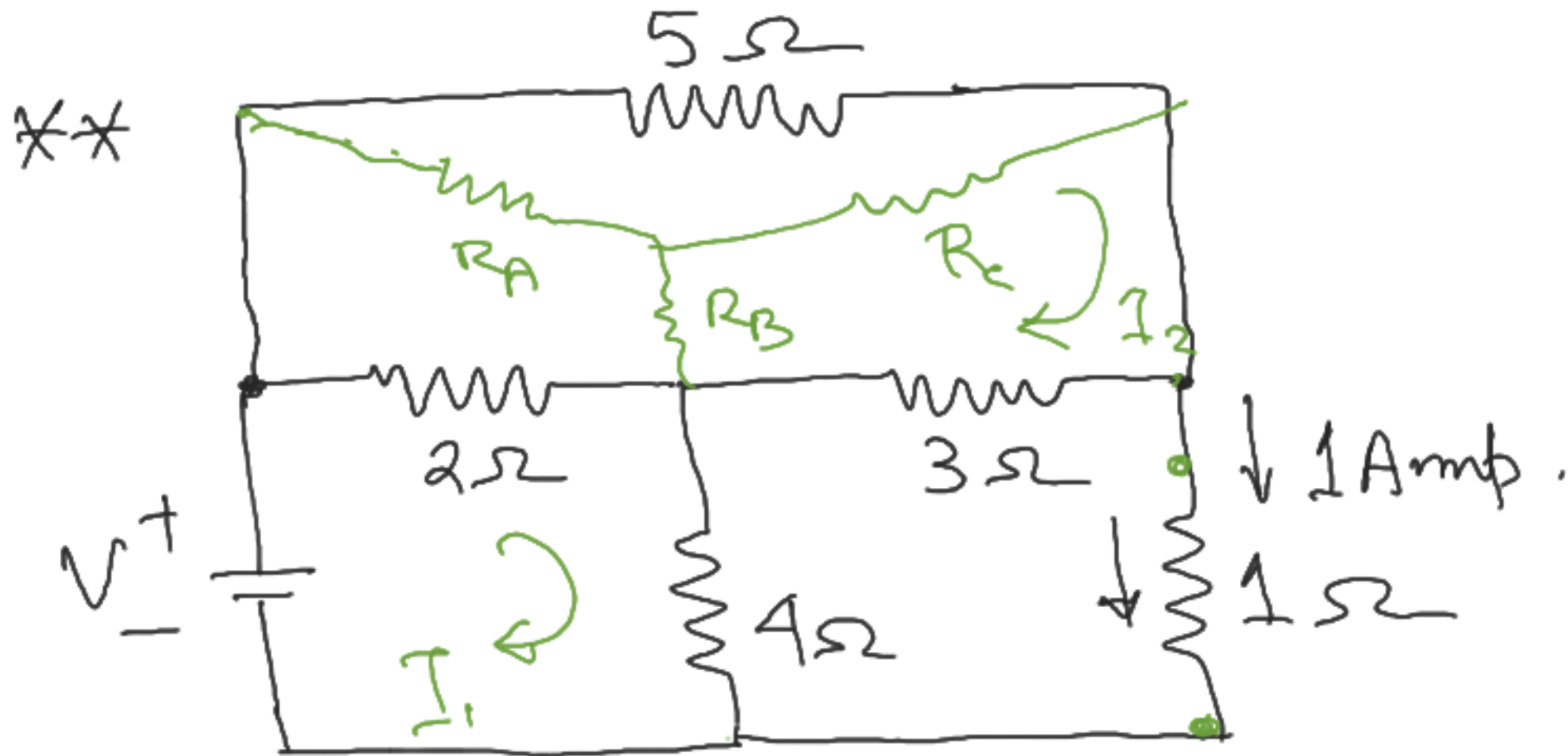
$$v = \frac{4}{9} \text{ Volt} \approx 0.44 \text{ volt}$$




$$R_A = 1\Omega$$

$$R_B = 0.6\Omega$$

$$R_C = 1.5\Omega$$


Find out V

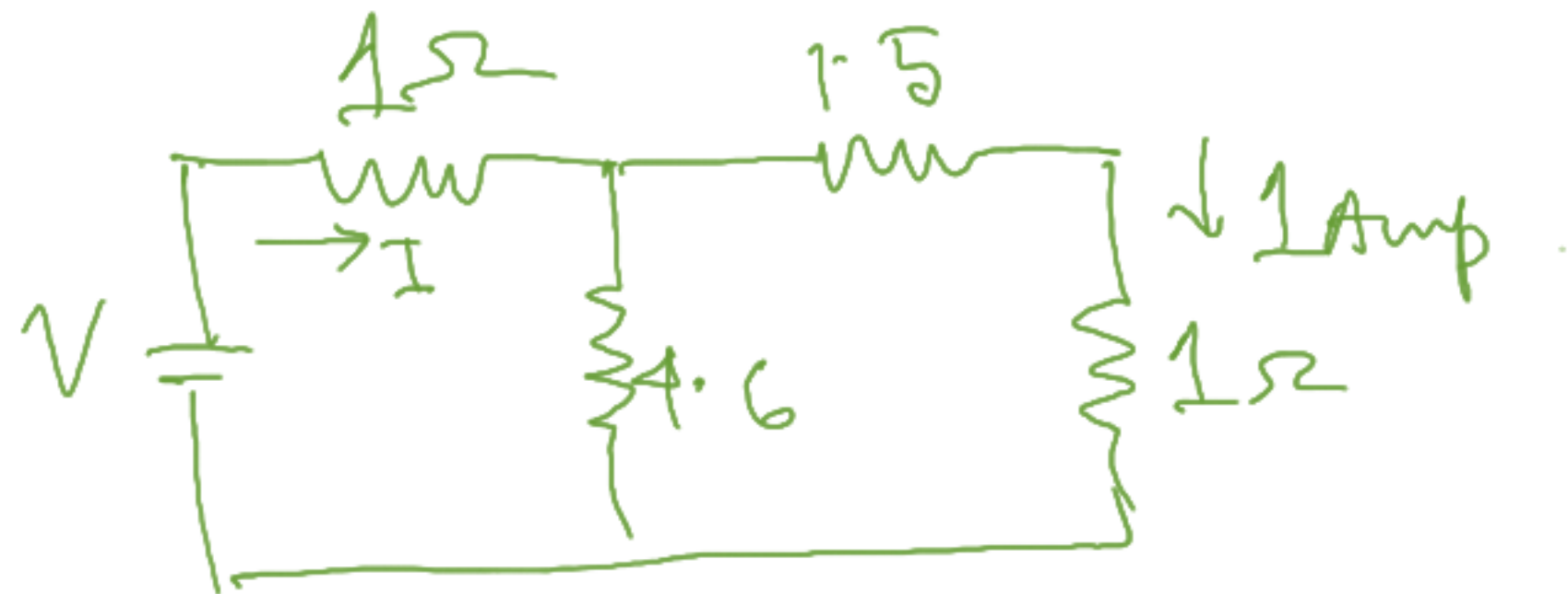

$$I = \frac{V}{R_{eq}}$$

$$1 = I \times \frac{4.6}{2.5 + 4.6} \Rightarrow 1 = \frac{V}{2.62} \times \frac{4.6}{2.5 + 4.6} \text{ or } V = 4.04 \text{ V}$$
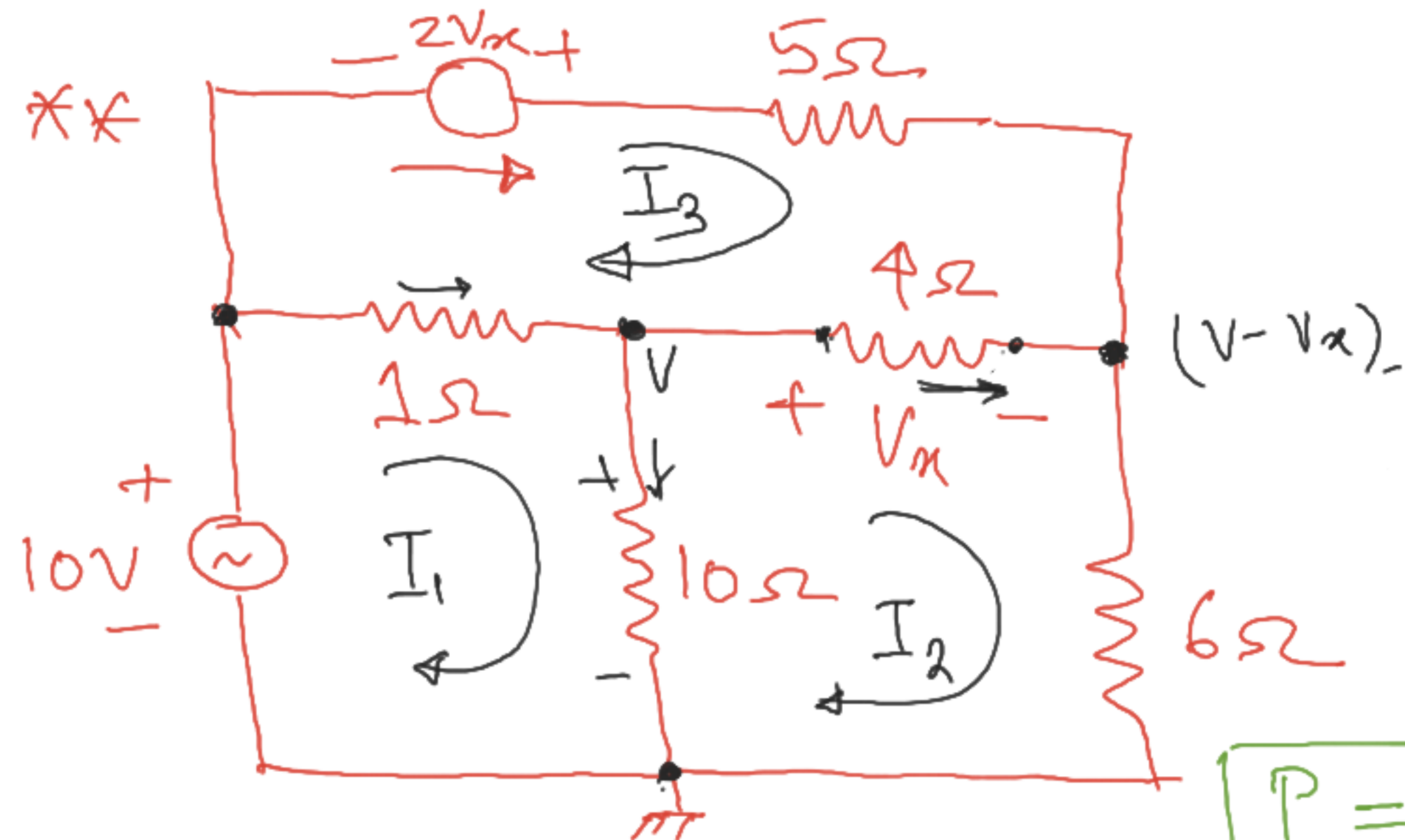
$$R_{eq} = 1 + \frac{2.5 \times 4.6}{2.5 + 4.6} = 2.62\Omega$$



$$V_x = (I_2 - I_3) \times 4 = -1.21 \text{ Volt}$$

$$I_1 = \frac{\Delta_1}{\Delta} = 2.36 \text{ Amp}$$

$$\Delta_1 = \begin{vmatrix} 10 & -10 & -1 \\ 0 & -20 & 4 \\ 0 & 12 & -18 \end{vmatrix} = 3432$$

$$P = 2 \times (-1.21) \times 0.964 = -2.33 \text{ Watt}$$

Find out the power delivered to the dependent voltage source.

$$I_2 = \frac{A_2}{\Delta} = 1.2767 \text{ Amp}$$

$$I_3 = \frac{A_3}{\Delta} = 0.964 \text{ Amp}$$

$$\begin{cases} 11I_1 - 10I_2 - I_3 = 10 \dots (i) \\ 10I_1 - 20I_2 + 4I_3 = 0 \dots (ii) \\ I_1 + 12I_2 - 18I_3 = 0 \dots (iii) \end{cases}$$

$$\Delta = \begin{vmatrix} 11 & -10 & -1 \\ 10 & -20 & 4 \\ 1 & 12 & -18 \end{vmatrix} = 1452$$